

ASSIGNMENT(PHYSICS)
CLASS-7
ELECTRICITY AND MAGNETISM

1. What do you mean by resistor?
2. Draw the circuit diagram of series combinations of resistors.