

Q1. What is a multiplexer?

Q2. How is multiplexer different from decoder?

Q3. Draw the circuit diagram for 8:1 multiplexer.