

Question 1.

- i)** What is Half-adder? Draw the truth table and write the Boolean expression for the sum and carry.
- ii)** Construct the logic circuit diagram for half-adder using only NAND gates.
- iii)** Construct the logic circuit diagram for half-adder using only NOR gates.