

Q1. What is an Encoder?

Q2. Draw the logic circuit diagram of :

- i. Hexadecimal to binary Encoder.
- ii. Base 4 to binary encoder.
- iii. Decimal to binary Encoder.