

Q1. Draw the logic circuit diagram of :

- i. Hexadecimal to binary Encoder.
- ii. Base 4 to binary encoder.
- iii. Decimal to binary Encoder.

[**Note:** Since no new topic was started, so practice the questions which were given in the previous assignment. In the next class, we shall learn about decoders. Thank you.]