

Q1. Explain the reduction procedure of a pair, quad and octet in K-map.

Q2. Reduce using K-map and draw the logic gate diagram for the reduced expression:

$$F(A,B,C,D) = \Sigma (0, 2, 4, 8, 9, 10, 12, 13)$$