

**Q1.** What is decoder? Explain.

**Q2.** Draw the logic circuit diagram of : 4 to 16 Decoder.