Question 1.

What is Full-adder? Explain the entire process to realize a Full-adder using two half-adder.